

Kirchhof Law

Input

Multiple test cases. For each test case:

The first line contains integers N and M ; N is a number of nodes in the circuit ($2 < N \leq 100$), M is the number of resistors ($0 \leq M \leq 300$). Each of the next M lines consists of three integers A_i , B_i and R_i — description of a resistor that has resistance R_i connecting the nodes A_i and B_i ($1 \leq A_i, B_i \leq N$; $1 \leq R_i \leq 100$).

There's a blank line between consecutive test cases in the input file. No other extra whitespace will/should be appear in the input/output.

Input terminates by EOF.

Output

For each test case, output the total resistance between the nodes 1 and N rounded within two digits after a decimal points. There won't be any test case the output for which is +INF.

Example

Input:

```
4 5
1 2 15
2 4 5
1 3 10
3 4 10
2 3 1
```

Output:

```
9.40
```